

1	(a)	$C = Q/V$ with symbols explained or charge per unit potential difference/voltage	1	[1]
	(b)	(i) (Electrons/negative) charge are/is moved from one plate of C to other plate (by the action of the battery) or battery sets up instantaneous current in circuit	1	
		(ii) $Q = CV = 500 \times 12 = 6000 \text{ } (\mu\text{C})$	1	[2]
	(c)	(i) Initial current = 6 mA; $R = V/I = 2 \times 10^3 \text{ } (\Omega)$ or finding $RC = 1.0 \text{ s}$; value of R	2	
		(ii) $RC = 1.0 \text{ (s)}$ ecf	1	
		(iii) $I = 6 \times (10^{-3}) e^{-t}$ ecf	1	
		(iv) Area under curve (is the integral of current against time/sum of $I \times \Delta t$ at all t); charge = current \times time / a mathematical link	2	
		(v) Initial current = 12 mA; curve with time constant = 0.5 s	2	[8]
		Total		11
2	(a)	(i) $E = V/d = 2000/4 \times 10^{-3} = 5 \times 10^5; \text{ N C}^{-1}/\text{V m}^{-1}$	2	2
		(ii) $Q = CV; = 200 \times 10^{-12} \times 2000; = 4 \times 10^{-7} = 0.40 \text{ } (\mu\text{C})$ taking p as 10^{-9} -1 mark/ correct conversion of any answer to μC gets final mark	3	3
		(iii) $W = \frac{1}{2} CV^2$ ecf possible = $\frac{1}{2} QV$; $= 0.5 \times 200 \times 10^{-12} \times 4 \times 10^6; = 400 \text{ } (\mu\text{J})$	1 2	 3
	(b)	(i) 4000 (V)	1	1
		(ii) 100 (pF) ecf from (b)(i)	1	1
		(iii) 800 (μJ) ecf from (b)(i),(ii) also accept twice (a)(iii)	1	1
	(c)	the mechanism pulling the plates apart/force working against attraction between charged plates/opposite charges/work done in separating plates/AW	1	1
		[Total]		12
3	(a)	(i) at least 3 parallel lines perpendicular to plates; arrows down	2	
		(ii) $V = Ed = 3 \times 10^5 \times 1.5 \times 10^3 = 450 \text{ M}/4.5 \times 10^8 \text{ (V)}$	1	
	(b)	battery acts as the (thermal) source of energy/models wind/AW; resistor required to model slow rate of charging of cloud (to 25 s)/AW; capacitor is the plates/cloud which become(s) charged;	1 1 1	
	(c)	(i) $I = Q/t; = 20/25 = 0.8 \text{ (A)}$	2	
		(ii) $R = V/I; = 4.5 \times 10^8/4.0 = 110\text{M}/1.1 \times 10^8 \text{ } \Omega$ ecf from c(i)	2	
		(iii) $C = Q/V; = 20/4.5 \times 10^8 = 4.4 \times 10^{-8}/44 \text{ n(F)}$	2	
		(iv) $T = RC; = 1.1 \times 4.4 = 4.95 \text{ or } 5.0\text{(s)}$ ecf from c(ii) & (iii)	2	
		Total		

4	a	i	$C_p = 2C + C = 3C$	1	
		ii	$1/C_s = 1/2C + 1/C ; = 3/2C$ giving $C_s = 2C/3$		2
	b	i	V	1	
		ii	$Q = C_p V ; = 3CV$ ecf from a(i)		2
	c		$E = \frac{1}{2} C_s V^2 ; = \frac{1}{3} CV^2$ ecf from a(ii)		2
	d	i	discharge circuit made through voltmeter/plates connected through voltmeter/AW	1	
			voltmeter behaves as a (large) resistor so plates will discharge;	1	
			rate of discharge depends on size of voltmeter's resistance/AW/		
			similar suitable comment	max 2	2
		ii	capacitors in series/Fig.4.2 as capacitance is smaller;	1	
			rate of discharge depends on value of RC/time constant	1	2
			Total		12
5	a		C = Q/V with symbols explained or charge per unit potential difference/voltage	1	
	b	i	$Q = CV ; = 4.7 \times 10^{-7} \times 11 = 5.2 \times 10^{-6}$ (C) or 5.2 (μ C)		2
		2	$E = \frac{1}{2} QV$ or $\frac{1}{2} CV^2 ; = 2.8(4) \times 10^{-5}$ (J) or 28.4 (μ J) possible ecf from b(i)		2
		ii	$V = IR ; I = 11/2200 = 5$ (mA) or 0.005 (A)		2
		2	$T = RC ; = 2200 \times 4.7 \times 10^{-7} = 1.0 \times 10^{-3}$ (s)		2
	c	i	attempt constant ratio for equal time intervals or other suitable method; achieved successfully	1	
				1	2
		ii	$\Delta Q = I \times \Delta t$; estimates area under graph between $t = 1$ ms and $t = 2$ ms;	2	
			$\Delta Q = 1.20 \pm 0.1 \times 10^{-6}$ (C) accept analytical answer using exp. function	1	3
			Total		14
6	a	i	$C = Q/V$ or gradient of graph / $= 24 \mu\text{C}/3\text{V} ; = 8.0$ (μ F)	2	
		ii	$E = \frac{1}{2} CV^2 / = \frac{1}{2} \times 8 \times 3^2 ; = 36$ (μ J) ecf a(i)	2	
			or $\frac{1}{2} QV / = \frac{1}{2} \times 24 \times 3 ; = 36$ (μ J)		
		iii	$T = RC = (0.04) ; R = 0.04/8.0\mu = 5.0 \times 10^3$ (Ω) ecf a(i)	2	
		iv	idea of exponential/constant ratio in equal times; which is independent of initial value/AW or argued mathematically in terms of $Q/Q_0 = e^{-t/RC}$ give 1 mark for statement that time depends only on time constant/RC	2	8
	b	i	$C_p = C + C = 6 \mu\text{F} ; 1/C_s = 1/2C + 1/C ; = 3/2C$ giving $C_s = 2C/3 = (2 \mu\text{F})$	3	
		ii	2 sets of (3 in series) in parallel/ 3 sets of (2 in parallel) in series	2	5
			Total		13
7	a	i	5.0 (V)	1	
		ii	10.0 (V)	1	2
	b	i	$Q = CV ; = 1.0 \times 10^{-3}$ (C)	2	
	b	ii	The total capacitance of each circuit is the same (namely 100 μ F) ; because capacitors in series add as reciprocals/ in parallel add/ supply voltage is the same and $Q = VC$, etc. max 2 marks	1	
				1	2
	c	i	A1 will give the same reading as A2; because the two ammeters are connected in series /AW	1	
			answer only in terms of exponential decrease for a maximum of 1 mark	1	
		ii	A4 will show the same reading as A2 at all times;	1	
			A3 will show half the reading of A2 initially; and at <u>all</u> subsequent times	2	5
			Total		11

8	a		$Q_0 = CV = 1.2 \times 10^{-11} \times 5.0 \times 10^3 ; = 6.0 \times 10^{-8} ; C$	3	3
	b	i	$RC = 1.2 \times 10^{15} \times 1.2 \times 10^{-11} \text{ or } = 1.44 \times 10^4 \text{ (s)}$	1	
		ii	$I = V/R = 5000/1.2 \times 10^{15} \text{ or } = 4.16 \times 10^{-12} \text{ (A)}$	1	
		iii	$t = Q_0/I ; = 6 \times 10^{-8} / 4.16 \times 10^{-12} = 1.44 \times 10^4 \text{ (s)}$	2	
		iv	$Q = Q_0 e^{-1} ; Q = 0.37 Q_0 \text{ so } Q \text{ lost} = 0.63 Q_0$	2	6
	c	i	capacitors in parallel come to same voltage	1	
			so Q stored \propto C of capacitor	1	
			capacitors in ratio 10^3 so only $10^{-3} Q_0$ left on football	1	
		ii	$V = Q/C = 6.0 \times 10^{-8} / 1.2 \times 10^{-8} \text{ or } 6.0 \times 10^{-11} / 1.2 \times 10^{-11} \text{ or only } 10^{-3}$ $Q \text{ left so } 10^{-3} V \text{ left; } = 5.0 \text{ (V)}$	2	5
	Total				14

9	a	i	$Q = VC ; W = \frac{1}{2} VC.V \text{ (} = \frac{1}{2} CV^2 \text{)}$	2	
		ii	parabolic shape passing through origin plotted accurately as $W = 1.1 V^2$	1	
				1	4
	b	i	$T = RC ; = 6.8 \times 10^3 \times 2.2 = 1.5 \times 10^4 \text{ s} = 4.16 \text{ h}$	2	
		ii	$\Delta W = \frac{1}{2} C(V_1^2 - V_2^2) = 1.1(25 - 16) ; = 9.9 \text{ (J)}$	2	
		iii	$4 = 5 \exp(-t/1.5 \times 10^4) ; \text{ giving } t = 1.5 \times 10^4 \times \ln 1.25 = 3.3 \times 10^3 \text{ (s)}$	2	
		iv	$P = \Delta W / \Delta t = 9.9 / 3.3 \times 10^3 = 3.0 \text{ mW}$ <i>ecf b(ii) and (iii)</i> <i>allow</i> $P = V_{av}^2 / R = 4.5^2 / 6.8 \times 10^3 = 2.98 \text{ mW}$	1	7
	Total				11

10	a	The charge flows one way/onto capacitor deflecting ammeter one way;		1	
		at discharge charge flows other way/off capacitor deflecting ammeter other way; or equal deflections at equal times from start of process; but in opposite directions or time constants same; currents opposite /AW		1	
					2
	b	$I_0 = 6.0 \times 10^{-4} ; V = I_0 R \text{ gives } 12 = 6.0 \times 10^{-4} \times R \text{ and } R = 2 \times 10^4 \Omega$		2	2
	c	i	current falls to $1/e$ (0.37) of initially chosen value in time constant; indication on graph, e.g. $I = 2.2 \times 10^{-4} \text{ A}$ at 5.0 s for initial current I_0	1	
				1	
	d	ii	$RC = 5.0 \text{ s ; so } C = (5.0/2.0) \times 10^{-4} \text{ (} = 2.5 \times 10^{-4} \text{ F)}$	2	4
		i	$Q = CV ; = 12 \times 250 \times 10^{-6} = 3.0 \times 10^{-3} \text{ C}$	2	
		ii	$I_0 t = 6.0 \times 10^{-4} \times 5.0 = 3.0 \times 10^{-3} \text{ C}$	1	
		iii	calculate the area under the graph (as $Q = It$)	1	4
	Total				12

11	a	i	9 V		1	
		ii	correct method, e.g same Q so $V = Q/C$ so larger C has half V of smaller one/ratio of V's inverse to C values		1	
	b	i	3 V		1	3
		ii	$Q = CV ; = 150 \times 9 = 1350 \text{ (}\mu\text{C)}$		2	
	c		$Q = CV = 150 \times 6 = 900 \text{ (}\mu\text{C)}$ <i>ecf (a)(ii)</i>		1	3
			$E = 1/2 CV^2$		1	
			in Fig. 5.1 $\frac{1}{2} \times 450 \times 9^2$		1	
			in Fig. 5.2 $\frac{1}{2} \times 100 \times 9^2$; so ratio f = 4.5		2	4
				Total		10

12	a	i	No charge on capacitor so held at 0 V	1	
			0 V across R means no current in A_1	1	2
		ii	12 V across 4.0 k Ω ; gives A_2 reading 3.0 mA	2	2
	b	i1	$A_1 = 2.0$ mA	1	
		2	$A_2 = 0$	1	2
		ii	potential divider argument or current in circuit is 2.0 mA so V across 2.0 k Ω is 4.0 V; capacitor in parallel or charged so draws no current/AW	1	
				1	2
		iii	$Q = CV$; $= 1 \times 10^{-3}$ C	2	2
	c	i	$A_1 = A_2 = 2.0$ mA	1	1
		ii	$RC = 0.5$ s	1	1
		iii	suitable scale and attempt at decay curve;	1	
			decay curve going through (0, 2); <i>ecf</i>	1	
			using $RC = 0.5$ s , e.g. passing through (0.5,0.735), (1.0,0.27), (1.5,0.1)	1	3
Total					15

13	(a)		$Q_0 = CV = 1.2 \times 10^{-11} \times 5.0 \times 10^3 ; = 6.0 \times 10^{-8};$ C	3	3
	(b)	(i)	$RC = 1.2 \times 10^{15} \times 1.2 \times 10^{-11}$ <i>or</i> $= 1.44 \times 10^4$ (s)	1	
		(ii)	$I = V/R = 5000/1.2 \times 10^{15}$ <i>or</i> $= 4.17 \times 10^{-12}$ (A)	1	
		(iii)	$t = Q_0/I ; = 6 \times 10^{-8} / 4.17 \times 10^{-12} = 1.44 \times 10^4$ (s)	2	
		(iv)	$Q = Q_0 e^{-1} ; Q = 0.37 Q_0$ so Q lost = $0.63 Q_0$	2	6
	(c)	(i)	capacitors in parallel come to same voltage so Q stored \propto C of capacitor capacitors in ratio 10^3 so only $10^{-3} Q_0$ left on plates	1 1 1	
		(ii)	$V = Q/C = 6.0 \times 10^{-8} / 1.2 \times 10^{-8}$ <i>or</i> $6.0 \times 10^{-11} / 1.2 \times 10^{-11}$ <i>or</i> only $10^{-3} Q$ left so 10^{-3} V left; $= 5.0$ (V)	2	5
			Total		14